 


2) 2 input NAND



(8, 8)

3) Based on the testbench

clk	D	Q^+
1	0	0
1	1	1
0	-	Q

$$Q^+ = D$$



glitch happen when the input make this transtation for \bar{Q} :

D=1, clk 0 to 1 : 8NS


4- active high reset

V1


V2

  


5-

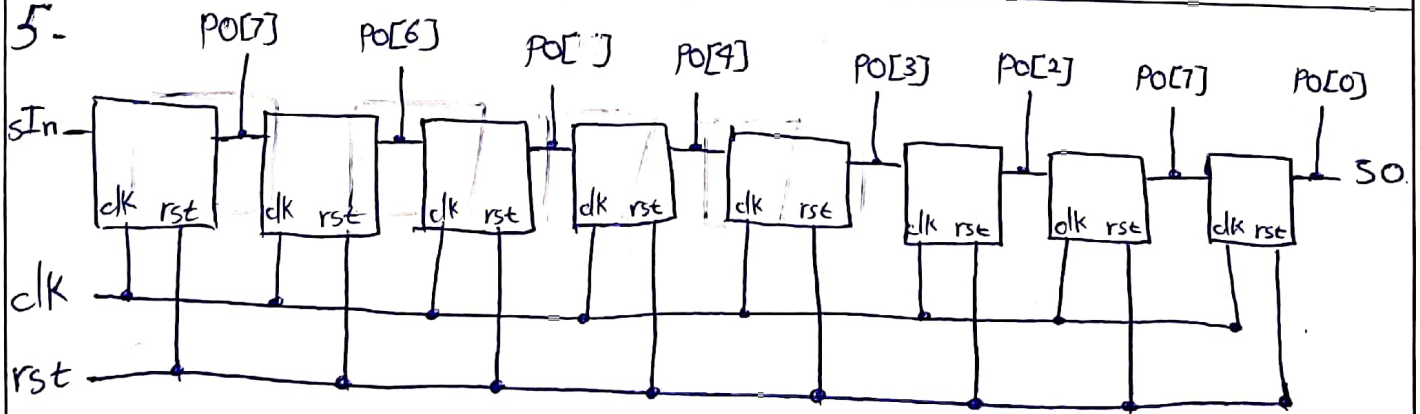

 6- The circuit of part 5 doesn't works as expected and the sIn will be shifted to all 8 bit output when we clk to 1 because we use D-Latch in this circuit and D-Latch have transparency.



8-a)

 

8-b) like part 5

9- like part 5

10 - Less logic block used

When we use always, we consider the worst case delay and we haven't any glitch.